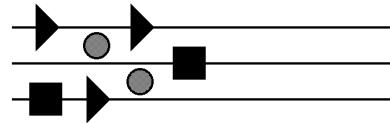






Integrated Circuits for Audio







drefahlaudio















peter drefahl







info@drefahlaudio.com



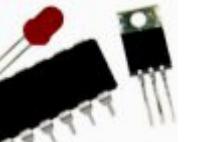
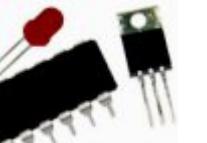
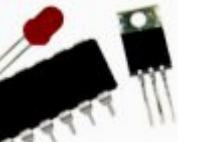
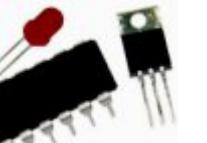
Semiconductors 	74HC165				8-bit shift register	B14	
Semiconductors 	8259AC-2				programmable interrupt controller	Bulk	
Semiconductors 	82C54				programmable timer	Bulk	
Semiconductors 	AD7225K N				quad DAC 8-bit	B14	

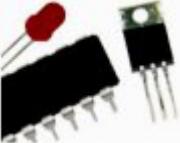
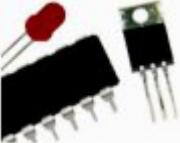
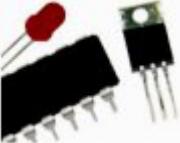
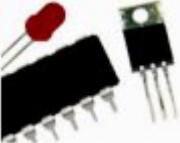
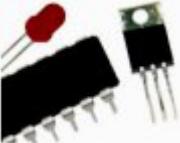
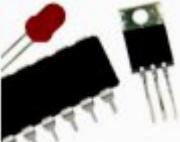
Semiconductors 	AM7202A					fifo memory 1024*9bit	B14	
Semiconductors 	BA6208					DC motor driver	B14	
Semiconductors 	DG211 CJ					quad analog switch	Bulk B14	
Semiconductors 	DG212 CJ					quad analog switch	Bulk	
Semiconductors 	DG408					analog multiplexer 1*8	Bulk	
Semiconductors 	GAL16V8- 25L					GAL	Bulk	

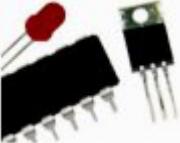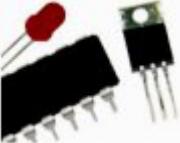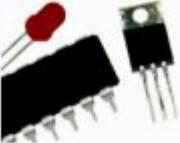
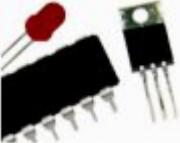
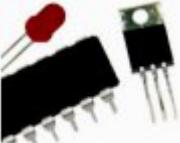
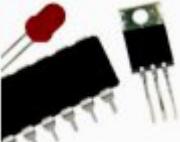
Semiconductors 	LF355					op-amp	B14	
Semiconductors 	LF355N					input op-amp	Bulk	
Semiconductors 	LF357 DP					low-noise/low-offset op-amp	B14	
Semiconductors 	LF357N					input op-amp	Bulk	
Semiconductors 	LM1972					2-channel audio attenuator with mute	Bulk	
Semiconductors 	LM1973					3-channel audio attenuator with mute	Bulk	

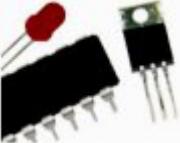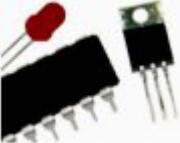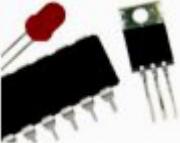
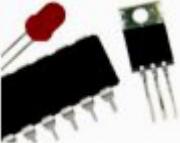
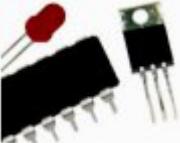
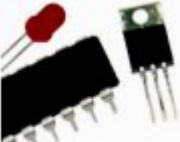
Semiconductors 	LM311N				voltage comparator	B14	
Semiconductors 	LM380N				audio amplifier 2,5W	Bulk	
Semiconductors 	MAX233 CPP				multichannel RS232 transceiver	Bulk	
Semiconductors 	MAX505 BCNG				DAC 8-bit	Bulk	
Semiconductors 	MAX690 CPA				microprocessor supervisory IC	Bulk	
Semiconductors 	MAX695 CPE				microprocessor supervisory IC	Bulk	

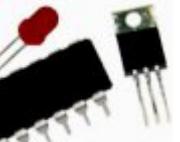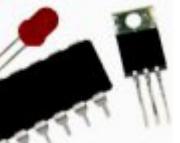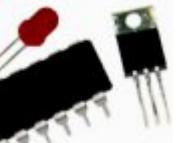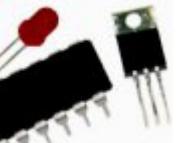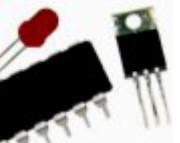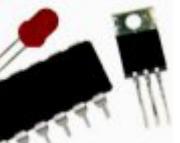Semiconductors 	MAX805L					microprocessor supervisory IC	Bulk	
Semiconductors 	MC1495CL					4-quadrant multiplier	Bulk	
Semiconductors 	MC34001					low-offset op-amp, 4MHz	B14	
Semiconductors 	MC34001					single input op-amp	Bulk	
Semiconductors 	PCF8582					EEprom 256 bytes	Bulk	
Semiconductors 	RC4739					OP vintage	B14	

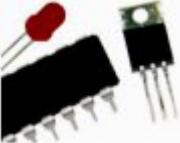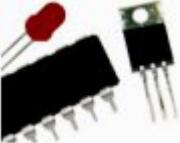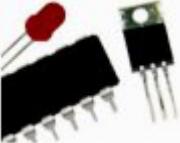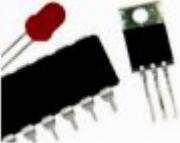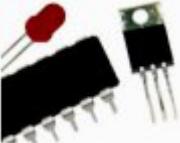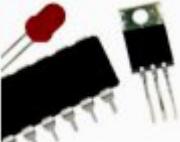Semiconductors 	Sanken SI 1010G				audio hybrid amp 10W	B14	
Semiconductors 	SCD551 0				LED alphanumeric line display	B14	
Semiconductors 	SSM2143				differential input amp -6dB	B14	
Semiconductors 	SSM2402				analog switch, dual	B14	
Semiconductors 	TC9142C				Quartz PLL motor controller	Bulk	
Semiconductors 	TD62083				Darlington driver	B14	

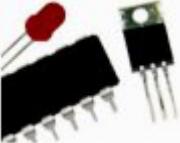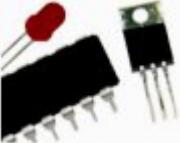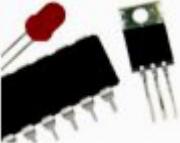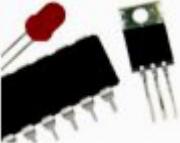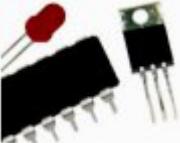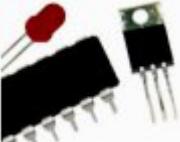Semiconductors 	TDA1054					preamp with auto level control ALC	Bulk	
Semiconductors 	TDA2030 H					HiFi amp, 14W	Bulk	
Semiconductors 	TL441CN					log. amplifier	Bulk	
Semiconductors 	TL7705 CP					voltage monitor	Bulk	
Semiconductors 	TLC0820					ADC 8-bit highspeed	B14	
Semiconductors 	TLC0820					ADC 8-bit	Bulk	

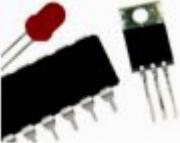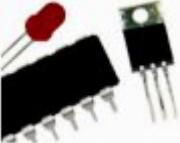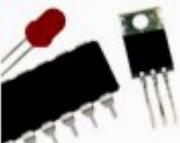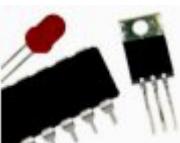Semiconductors 	TLC7528				DAC, 8-bit, multiplying	Bulk	
Semiconductors 	U237 BGA	TFK			5-segment LED meter, lin. combines with U247 for 10 LEDs	Bulk	
Semiconductors 	U247 BGA	TFK			5-segment LED meter, lin. combines with U237 for 10 LEDs	Bulk	
Semiconductors 	U257	TFK			5-segment LED meter, log. combines with U267 for 10 LEDs	Bulk	
Semiconductors 	U267	TFK			5-segment LED meter, log. combines with U257 for 10 LEDs	Bulk	
Semiconductors 	UAA170				16-segment LED meter	Bulk	

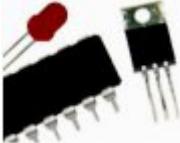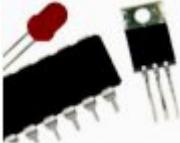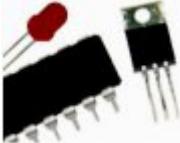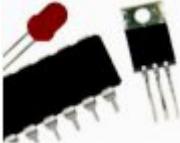Semiconductors 	ULN2003					7-channel driver for fader motors	Bulk	
Semiconductors 	ULN2004 AN					7-channel driver for fader motors	Bulk	
Semiconductors 	ULN2803					Darlington driver octal	B14	
Semiconductors 	XR2206					function generator sine/saw/square	B14	

End of listing